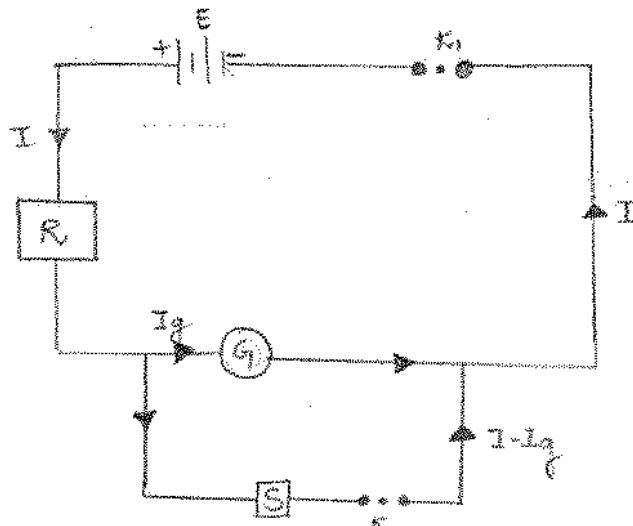


Index

Sr. No	Name of the Experiment	Page No.	Date of Experiment	Date of Submission	Remarks
1.	TO DETERMINE RESISTANCE OF GALVANOMETER BY HALF DEFLECTION METHOD.	1.	08/04/13		✓
2.	TO DETERMINE RESISTANCE OF GIVEN WIRE USING OHM'S LAW	2.	01/07/13		✓
3.	METRE BRIDGE	3.	02/07/13		✓
4.	METRE BRIDGE	4.	09/07/13		✓
5.	MINIMUM DEVIATION FOR PRISM	5.	16/07/13		✓
6.	TRAVELLING MICROSCOPE	7.	23/07/13		✓
7.	I-V CHARACTERISTICS OF P-N JUNCTION IN FORWARD BIAS	8.	30/07/13		✓
8.	I-V CHARACTERISTICS OF P-N JUNCTION IN REVERSE BIAS	9.	06/08/13		✓
9.	FOCAL LENGTH OF CONCAVE MIRROR	10.	20/08/13		✓
10.	FOCAL LENGTH OF CONVEX LENS	11.	27/08/13		✓
11.	FOCAL LENGTH OF CONCAVE LENS	13.	03/09/13		✓
12.	CHARACTERISTICS OF A ZENER-DIODE	15.	10/09/13		✓
13.	ACTIVITY 1	16.	17/09/13		✓
14.	ACTIVITY 2	17.	18/09/13		✓
15.	ACTIVITY 3	18.	24/09/13		✓
16.	ACTIVITY 4	19.	25/09/13		✓
17.	ACTIVITY 5	20.	1/10/13		✓
18.	ACTIVITY 6	21.	2/10/13		✓
19.	ACTIVITY 7	22.	7/10/13		✓



RESISTANCE OF GALVANOMETER

OBSERVATION

S.NO	RESISTANCE(R)	Deflection in G (θ)	Shunt Resistance (S) θ _g	Half Deflection (θ/2)	G = $\frac{R_s}{R+R_s}$
1.	7000	22	47	11	47.2.2
2.	6200	26	47	13	47.2.2
3.	9000	18	47	9	47.2.2
4.	10000	16	47	8	47.2.2
5.	8000	20	47	10	47.2.2

CALCULATION

$$G = G_1 + G_2 + G_3 + G_4 + G_5$$

$$= 5 \times 47.2 \Omega$$

$$G = 47.2 \Omega$$

TO DETERMINE RESISTANCE OF A GALVANOMETER BY HALF DEFLECTION METHOD

AIM: To determine resistance of a galvanometer by half deflection method

APPARATUS: A weston type galvanometer, a voltmeter, battery, resistance boxes ($10,000\ \Omega$ and $200\ \Omega$), keys, rheostat, metre scale, ammeter, wires, sand paper.

THEORY: The resistance of the given galvanometer is given by

$$\frac{G}{R-S} = \frac{R}{S}$$

(R = resistance in series)
(S = shunt resistance)

RESULT: Resistance of the given galvanometer = $47.2\ \Omega$

PRECAUTIONS:

1. All connections should be neat, clean and tight.
2. All plugs in resistance boxes must be tight.

SOURCES OF ERROR:

1. The screws of the instrument may be loose.
2. The plugs of resistance boxes may not be clean.

Teacher's Signature :

SCALE
Y - AXIS UNIT = 0.05A
X - AXIS UNIT = 0.1V

TANG. X A = 0.2 - 0.1 = 0.1
BC = 0.1 - 0.05 = 0.05

Resistance $R = \rho L / A$ (17)

$$R = 0.6 \times 10^{-2} \Omega \text{ cm}$$

X = 34.5

(0.1, 0.05)

(0.2, 0.1)

(0.3, 0.15)

(0.25, 0.1)


(0.25, 0.05)

(0.2, 0.2)

POTENTIAL DIFFERENCE (V)

0 0.05 0.1 0.15 0.2 0.25 0.3 0.35 0.4 0.45 0.5 0.55 0.6 0.65 0.7 0.75

CURRENT (AMPERE)

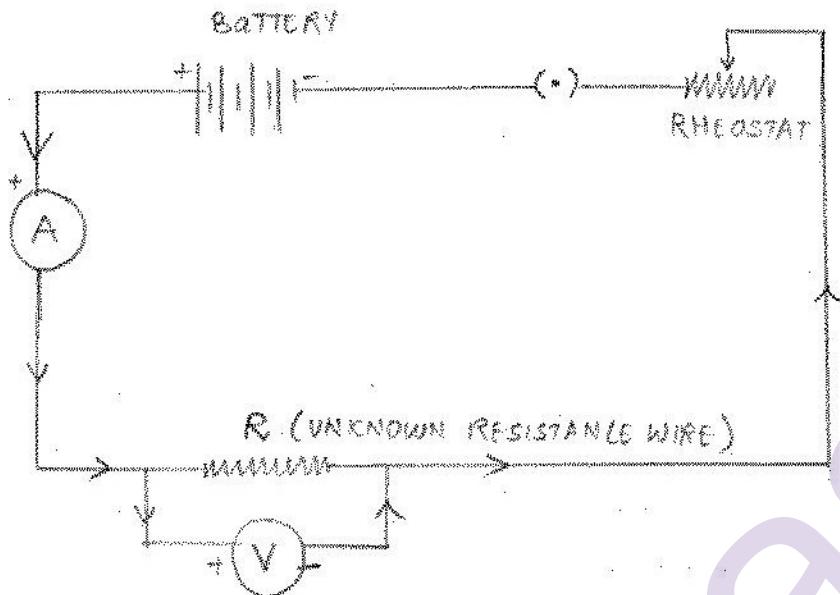

OBSERVATIONS

- 1) Length of wire = 36.5 cm
- 2) Range of Ammeter : 0-3 A
- 3) Range of Voltmeter : 0-5 V

Least count: 0.05 A

Zero error: nil

Least count: 0.1 V

Zero error: nil

S.NO	VOLTMETER Reading	AMMETER Reading	$\frac{V}{I} = R \Omega$
1.	0.3 V	0.35 A	0.9-2
2.	0.4 V	0.40 A	1-2
3.	0.5 V	0.55 A	0.9-2
4.	0.7 V	0.70 A	1-2

$$R_{\text{net}} = R_1 + R_2 + R_3 + R_4 \approx 0.95 \Omega$$

$$\frac{R}{l} \Rightarrow \frac{0.95}{36.5} \Rightarrow 2.603 \times 10^{-2} \Omega \text{ cm}^{-1}$$

TO DETERMINE RESISTANCE PER UNIT LENGTH OF A GIVEN WIRE USING OHM'S LAW

AIM: To determine resistance per cm of a given wire by plotting a graph of potential difference versus current.

REQUIREMENTS: A resistance wire, a voltmeter, ammeter, battery, rheostat, meter scale, connecting wires and key.

THEORY: According to ohm's law

$$\begin{aligned} V &\propto I \\ \Rightarrow V &= IR \\ &\qquad\qquad\qquad V = \text{Potential difference} \\ &\qquad\qquad\qquad I = \text{current} \\ &\qquad\qquad\qquad R = \text{Resistance} \end{aligned}$$

$$\frac{V}{I} = R$$

R depends on nature of material, temp and dimensions.

RESULT: (i) Resistance per cm of the wire is $2.603 \times 10^{-2} \Omega \text{ cm}^{-1}$
(ii) The graph between V and I is a straight line


PRECAUTIONS:

- 1) The connections should be neat, clean and tight.
- 2) Voltmeter and ammeter should be of proper range.

SOURCES OF ERROR:

- 1) The instrument screws may be loose.
- 2) Rheostat may have high resistance.

Teacher's Signature :

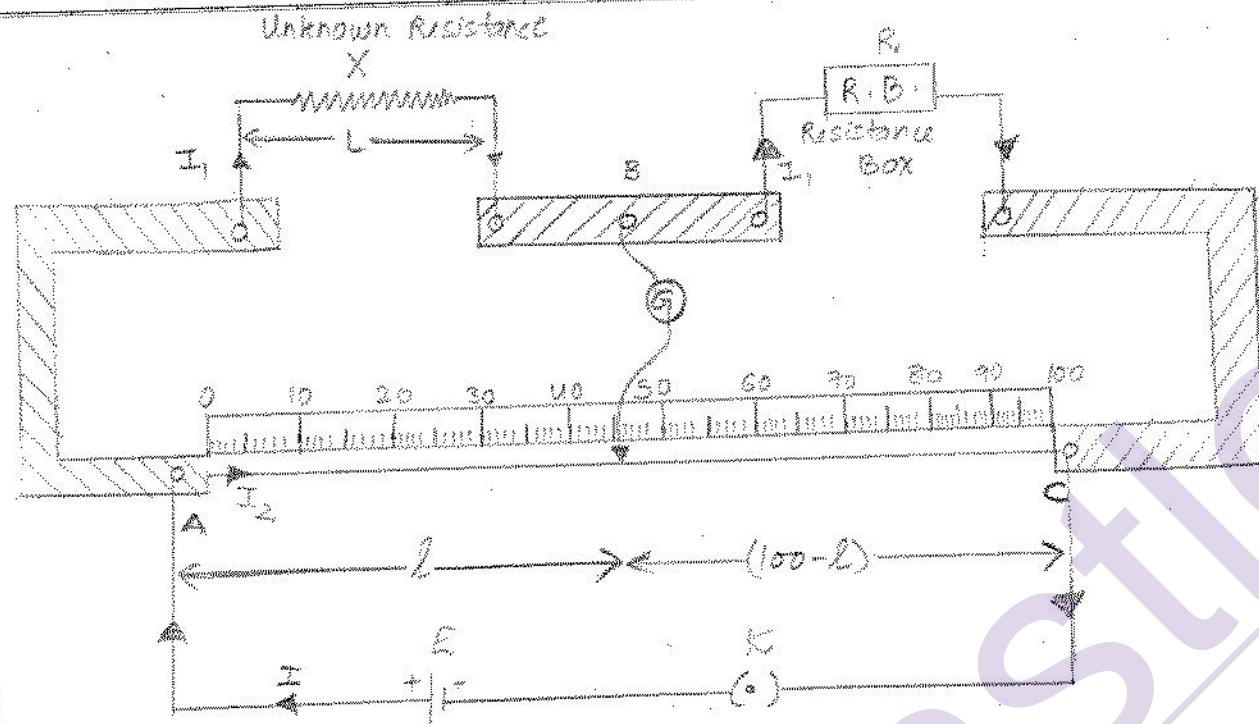

OBSERVATIONS

- 1) length of wire = 300cm
- 2) diameter of wire = 0.025 cm last count of screw gauge: 0.001

S.No	Resistance	$l\text{ (cm)}$	$100-l\text{ (cm)}$	$X = \frac{l}{100-l} \times R$
1.	4.24	37.4 cm	62.6 cm	4.24 - 2
2.	4.31	53.7 cm	46.3 cm	4.31 - 2
3.	4.57	68.6 cm	31.4 cm	4.57 - 2

3) Mean Resistance of wire = (\bar{X}) = 4.44 - 2

4) Resistivity = $\frac{X \pi D^2}{4l}$ = $7.26 \times 10^{-7} \Omega m$

Expt. No. 3

METRE BRIDGE

AIM: To find resistance of a given wire using metre bridge and hence determine the specific resistance of its material.

APPARATUS: A meter bridge, battery, Θ , resistance box, jockey, resistance wire, screw gauge, metre scale, connecting wires.

THEORY: Formula used

1) Unknown Resistance X is given by

$$\frac{X}{100-l} = \frac{l}{X_R}$$

2) Specific Resistance is given by

$$\rho = \frac{X \pi D^2}{4L}$$

RESULT: 1) The value of unknown resistance X =

2) Specific resistance of the unknown wire is =



PRECAUTIONS:

1. All connections should be neat, clean and tight.
2. All the plugs in the resistance box should be tight.

SOURCES OF ERROR:

1. The instrument screws may be loose.
2. The plugs may not be clean.

Teacher's Signature : goh

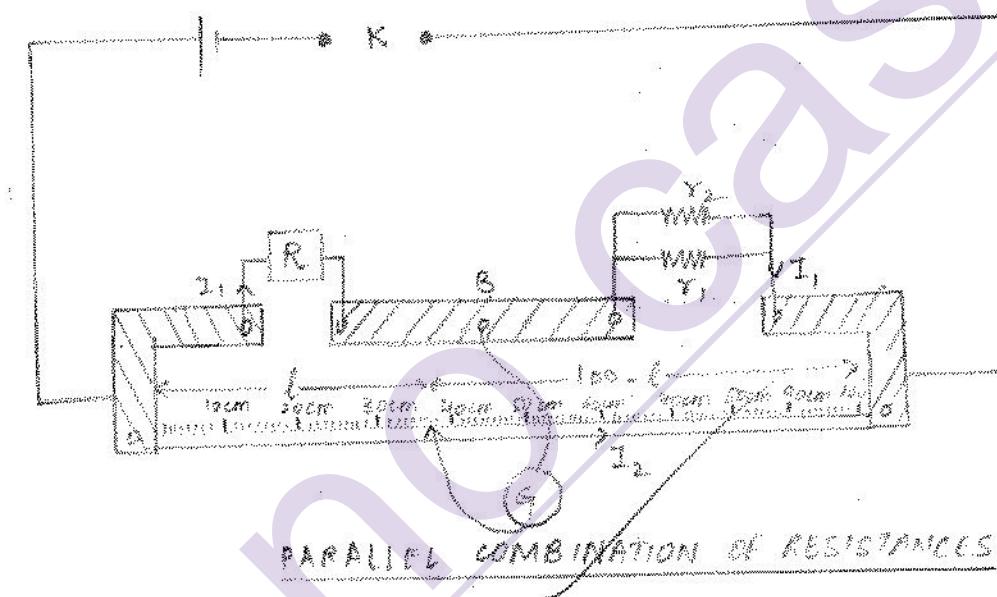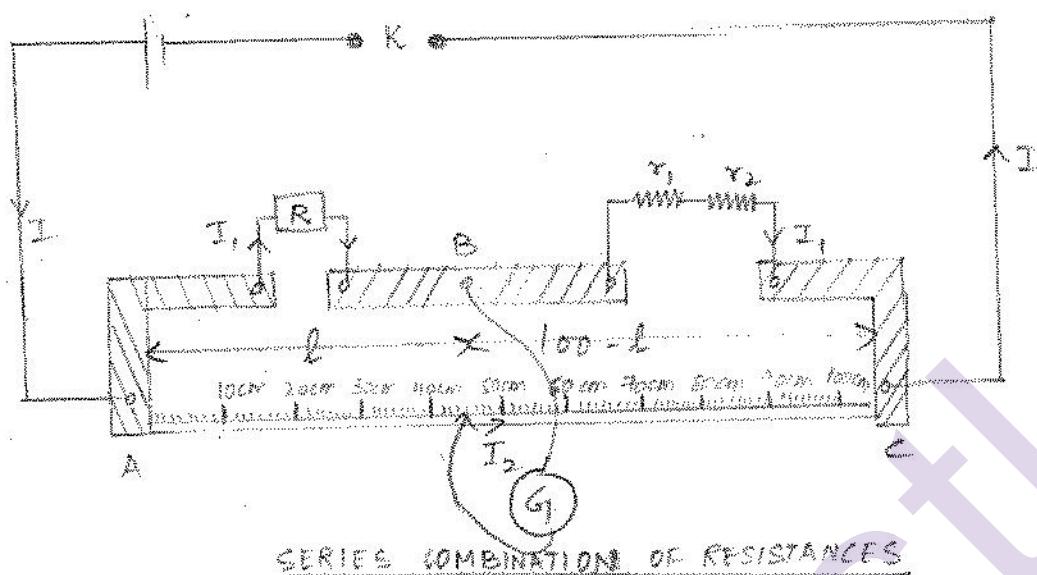

RESISTANCE COIL	No. of PBS	R Ω	L cm	H00 - Dcm	r = (H00 - D) / 2	Mean resistance	Mean Resist. force	THEORETICAL VAL
T ₁ only	1	5.2	31 cm	29 cm	1.97 Ω	T ₁ = 1.98 Ω	T ₁ = 2.52	
	2	5.2	31.2 cm	28.8 cm	1.95 Ω			
	3	5.2	31.6 cm	28.4 cm	1.95 Ω			
T ₂ only	1	3.5	35 cm	26 cm	0.95 Ω	T ₂ = 1.2	T ₂ = 1.0	
	2	3.2	36.2 cm	23.8 cm	1.1 Ω			
	3	3.2	37.4 cm	26 cm	1.1 Ω			
T ₁ + T ₂ = 8	1	7.2	69 cm	31 cm	2.3 Ω	R _g = 2.94 Ω & R _t = 3.2		
	2	7.2	70 cm	30 cm	3.0 Ω			
	3	7.2	68 cm	32 cm	3.1 Ω			
R _p = T ₁ + T ₂	1	9.2	95 cm	7 cm	6.65 Ω	R _p = 0.61 Ω	R _p = 0.66 Ω	
	2	9.2	92.7 cm	6.3 cm	0.62 Ω			
	3	9.2	91 cm	4.5 cm	0.59 Ω			

METRE BRIDGE

AIM: To verify the laws of combination (series and parallel) of resistances using a metre bridge.

APPARATUS: A metre bridge, battery, a (G) , resistance box, jockey, resistance coils, connecting wires, sand paper.

THEORY: (i) Unknown resistance = $\left| \frac{(100-l) \times R}{l} \right|$

(ii) $R_s = Y_1 + Y_2$

(iii) $R_p = \frac{Y_1 Y_2}{Y_1 + Y_2}$

RESULT:


- 1) Within limits of experimental error, experimental and theoretical values of R_s are same. Hence, law of resistances in series is verified.
- 2) Within limits of experimental error, experimental and theoretical values of R_p are same. Hence, law of resistance in parallel is verified.

PRECAUTIONS: 1) All connections should be clean, neat and tight.
2) All the plugs in the resistance should be tight.


SOURCES OF ERROR:




- 1) The instrument screws may be loose.
- 2) The plugs may not be clean.


Teacher's Signature :

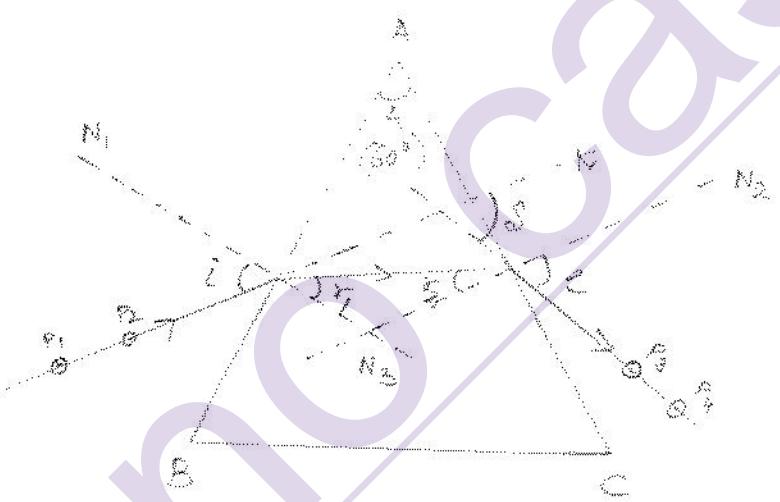

S.NO	ANGLE OF INCIDENCE (°)	ANGLE OF DEVIATION (°)
1.	35°	44°
2.	40°	33.9°
3.	45°	29°
4.	47.5°	34.5° (S)
5.	50°	38.5°
6.	55°	40°

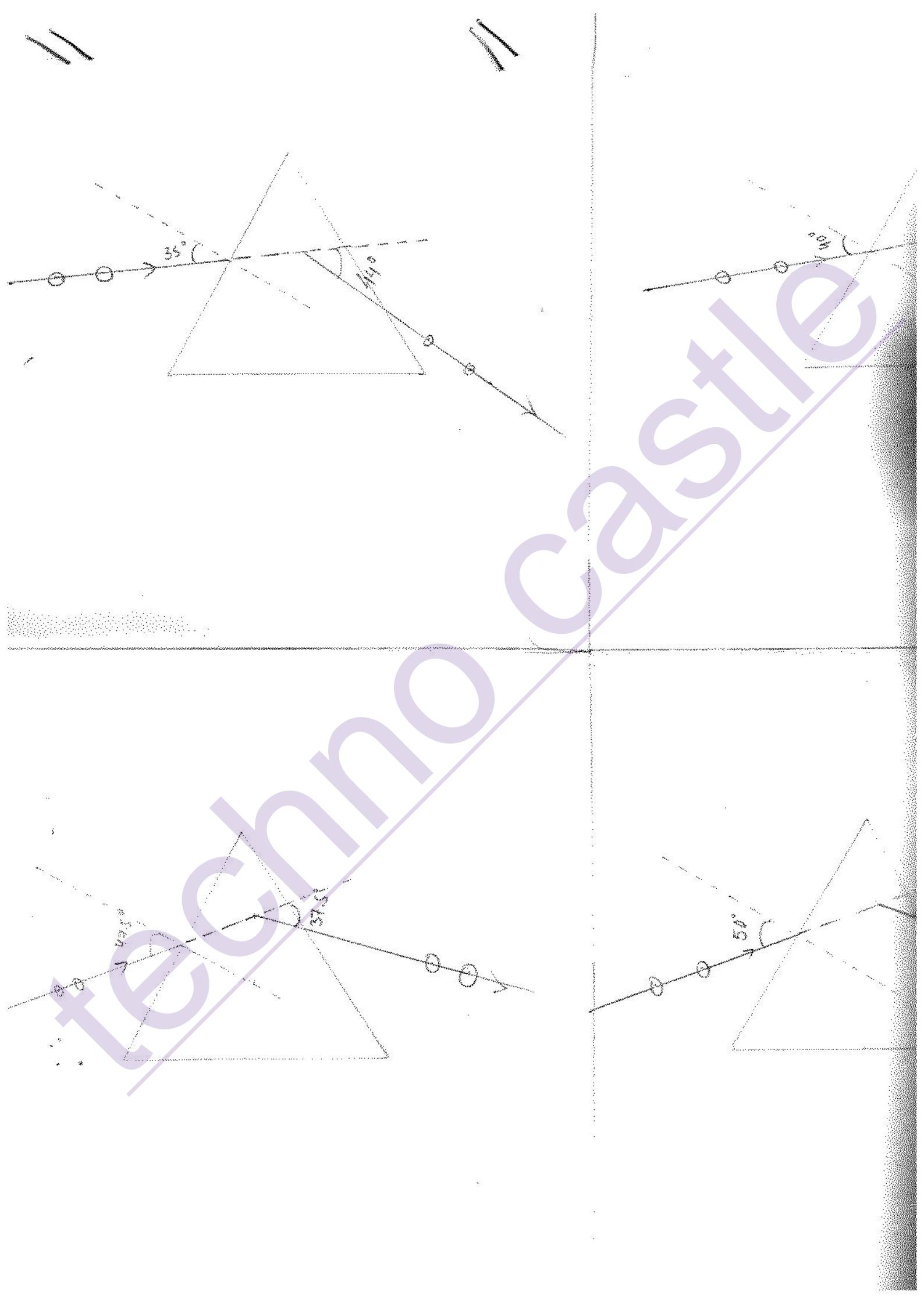

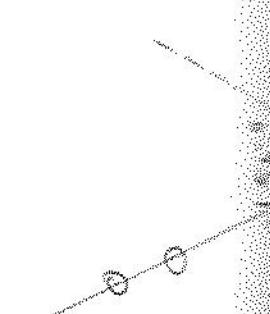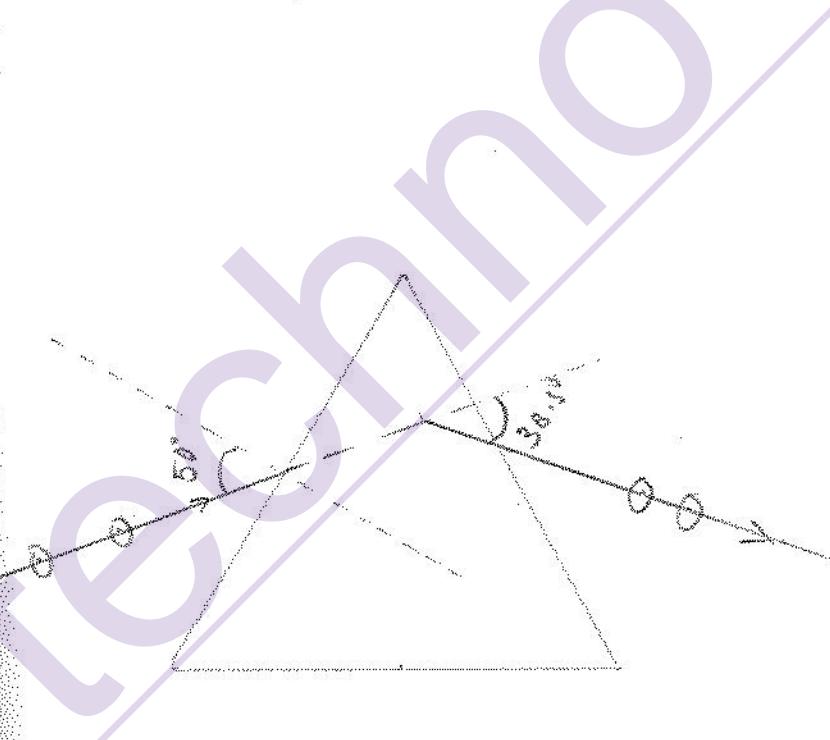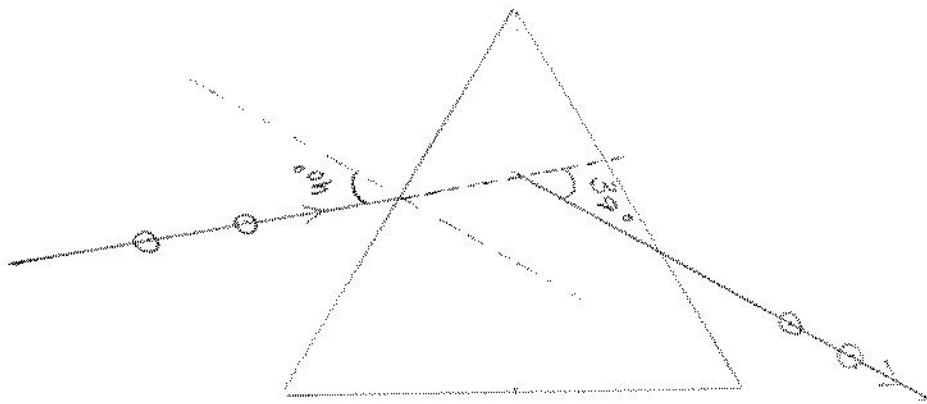

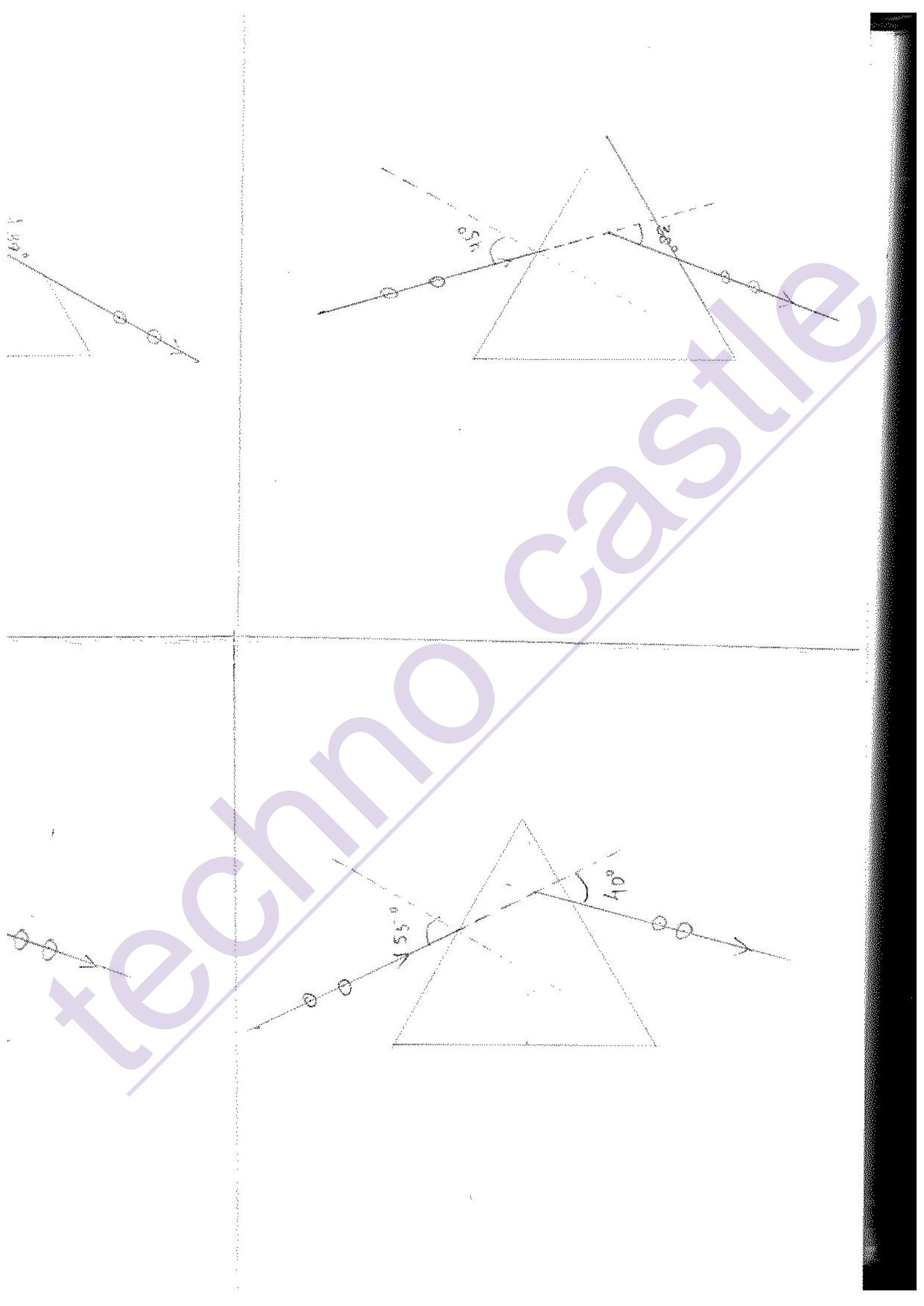

techno castle

ANGLE OF MINIMUM DEVIATION

AIM: To determine angle of minimum deviation for a given prism by plotting a graph between angle of incidence and angle of minimum deviation.

APPARATUS: Drawing board, white sheet of paper, prism, drawing pins, pencil, metre scale, office pins, graph paper, protractor.

THEORY: The refractive index (μ) of a material is given by

$$\mu = \frac{\sin (A + S_m)}{2}$$

$$\frac{\sin (A)}{2}$$

S_m = angle of minimum deviation

A = angle of prism

RESULT:

- (i) I-S graph indicates that as angle of incidence (i) increases, angle of deviation (D) first decreases, attains a minimum value (S_m) and then starts increasing for further increase in angle of incidence.
- (ii) angle of minimum deviation $S_m = 37.5^\circ$
- (iii) Refractive index of prism (μ) = 1.567


Teacher's Signature : _____

GRAPH BETWEEN i and s

Scales

X axis 9 cm = 5°

Y axis 8 cm = 5°

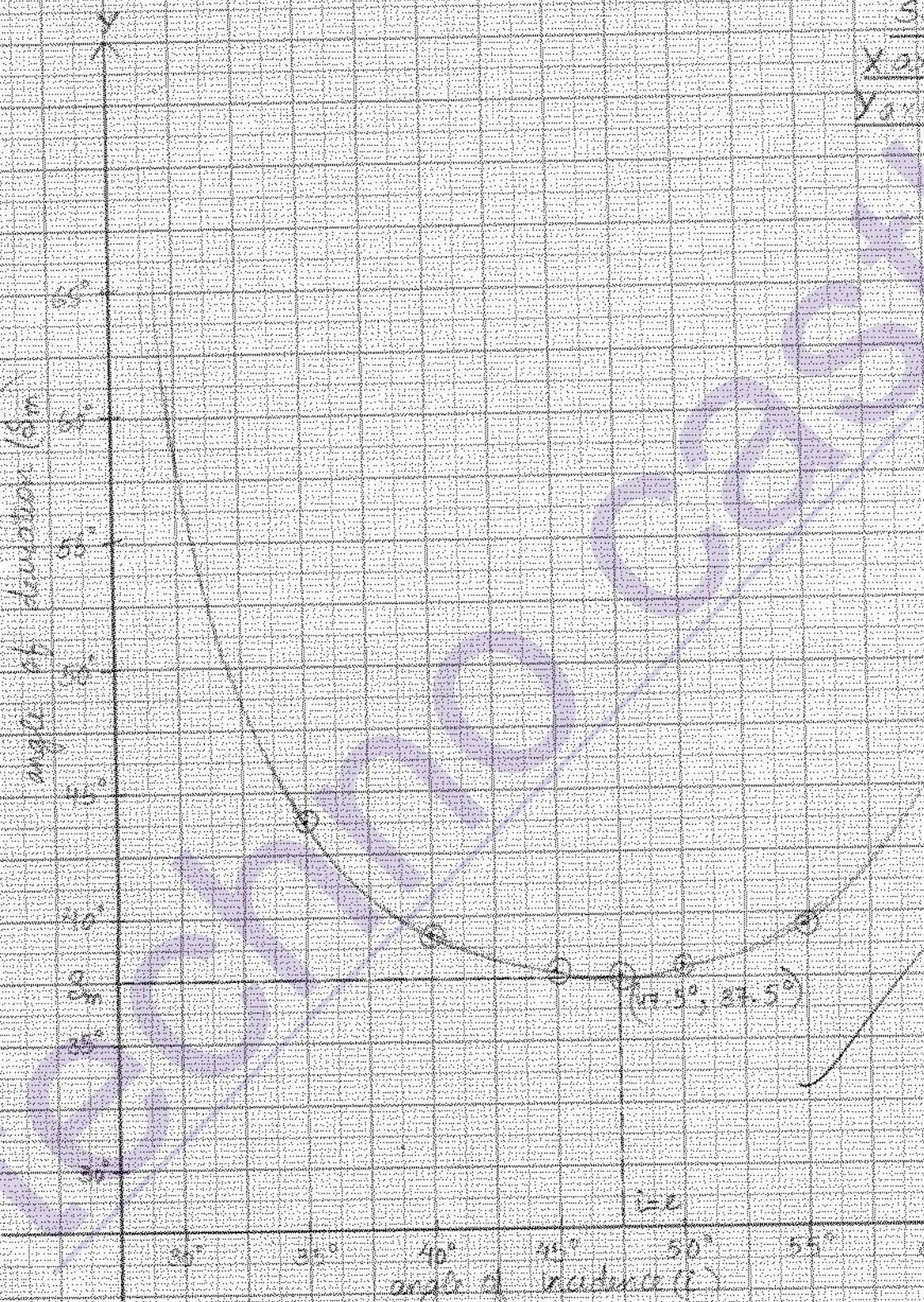

PRECAUTIONS:

- 1) angle of incidence lies between $35^\circ - 60^\circ$
- 2) pins should be fixed vertical
- 3) The same angle of prism should be used for all observations

SOURCES OF ERROR

- 1) Pin pricks may be thick
- 2) measurement of angles may be wrong



Teacher's Signature :

SERIAL NO	READING ON VERTICAL SCALE WHEN MICROSCOPE IS FOCUSED ON			REAL THICKNESS $R_3 - R_1$ (cm)	APPARENT THICKNESS $R_3 - R_2$ (cm)	$\mu = R_2 - R_1$ $R_3 - R_2$
	CROSS MARK WITHOUT SLAB (R ₁)cm	CROSS MARK WITH SLAB (R ₂)cm	Lycopodium POWDER (R ₃)cm			
1.	0cm	0.39cm	1.2cm	1.2cm	0.81cm	1.5
2.	0.4cm	0.40cm	1.23cm	1.23cm	0.83cm	1.48
3.	0cm	0.41cm	1.19cm	1.19cm	0.78cm	1.52

$$\mu = \frac{N_1 + N_2 + N_3}{3}$$

$$= \frac{1.5 + 1.48 + 1.52}{3}$$

3

$$= \frac{4.5}{3}$$

$$\boxed{\mu = 1.5}$$

TRAVELLING MICROSCOPE

AIM: To determine refractive index of a glass slab, using travelling microscope.

APPARATUS: glass slab, a travelling microscope, lycopodium powder,

THEORY:

$$\mu_g = \frac{\text{real thickness of slab}}{\text{apparent thickness of slab}}$$

RESULT:

$$\frac{\text{The ratio of } R_3 - R_1}{R_3 - R_2} \text{ is constant}$$

It gives the refractive index of glass slab
Refractive index of glass slab is 1.5

PRECAUTIONS:

- i) In microscope, the parallax should be properly removed
- ii) The microscope should be moved in upper direction only to avoid back lash error

SOURCES OF ERROR:

- i) The microscope scale may not be properly calibrated


Teacher's Signature : _____

Range of VOLTMETER: 0-3V
 Least count of voltmeter: 0.1V
 Range of AMMETER: 0-50mA
 Least count of ammeter: 1mA

S.NO	FORWARD VOLTAGE	FORWARD CURRENT
1.	0V	0mA
2.	0.1V	0mA
3.	0.3V	0mA
4.	0.4V	0.5mA
5.	1.2	5mA
6.	1.6	10mA
7.	1.8	15mA
8.	2	20mA
9.	2.2	25mA
10.	2.4	30mA

$$\Delta V = (2 \text{ to } 3) = 0.4V \quad \Delta I_F = 10mA$$
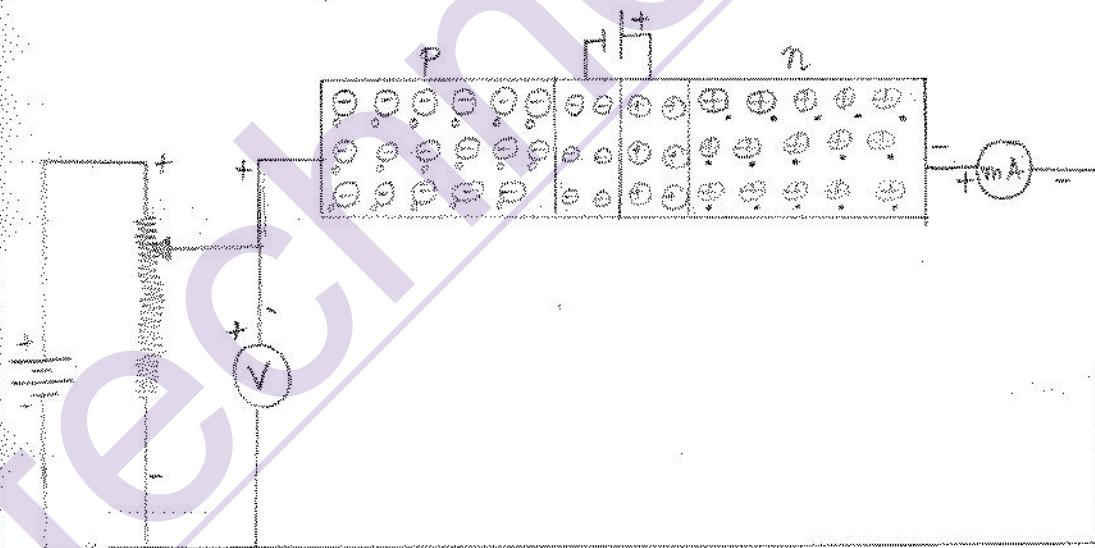
$$R = \frac{V}{I} = \frac{\Delta V}{\Delta I_F} = \frac{0.4 \times 10^3}{10} = 40\Omega$$



P-N-JUNCTION UNDER FORWARD BIAS

AIM: To draw I-V characteristics curve of a p-n-junction in forward bias.

APPARATUS: A p-n diode, a 3-volt battery, a 50 volt battery, a high resistance, rheostat, 0-3V voltmeter, 0-50V voltmeter, 0-100mA ammeter, one way key, connecting wires, sand paper.

THEORY: Forward-bias characteristics: When the p-section of the diode is connected to +ve terminal of a battery and n-section to -ve terminal of battery it is said to be forward biased.

With increase in voltage, the forward current increases slowly in the beginning and then rapidly at 0.7V for si diode. Current increases rapidly. This is called threshold voltage.

RESULT:

Junction resistance in forward bias = 40 ohms


PRECAUTIONS:


- 1) All connections should be neat, clean and tight.
- 2) Key should be used in circuit and opened when circuit is not used.

SOURCES OF ERROR:

- 1) The junction diode supplied may be faulty.

Teacher's Signature :

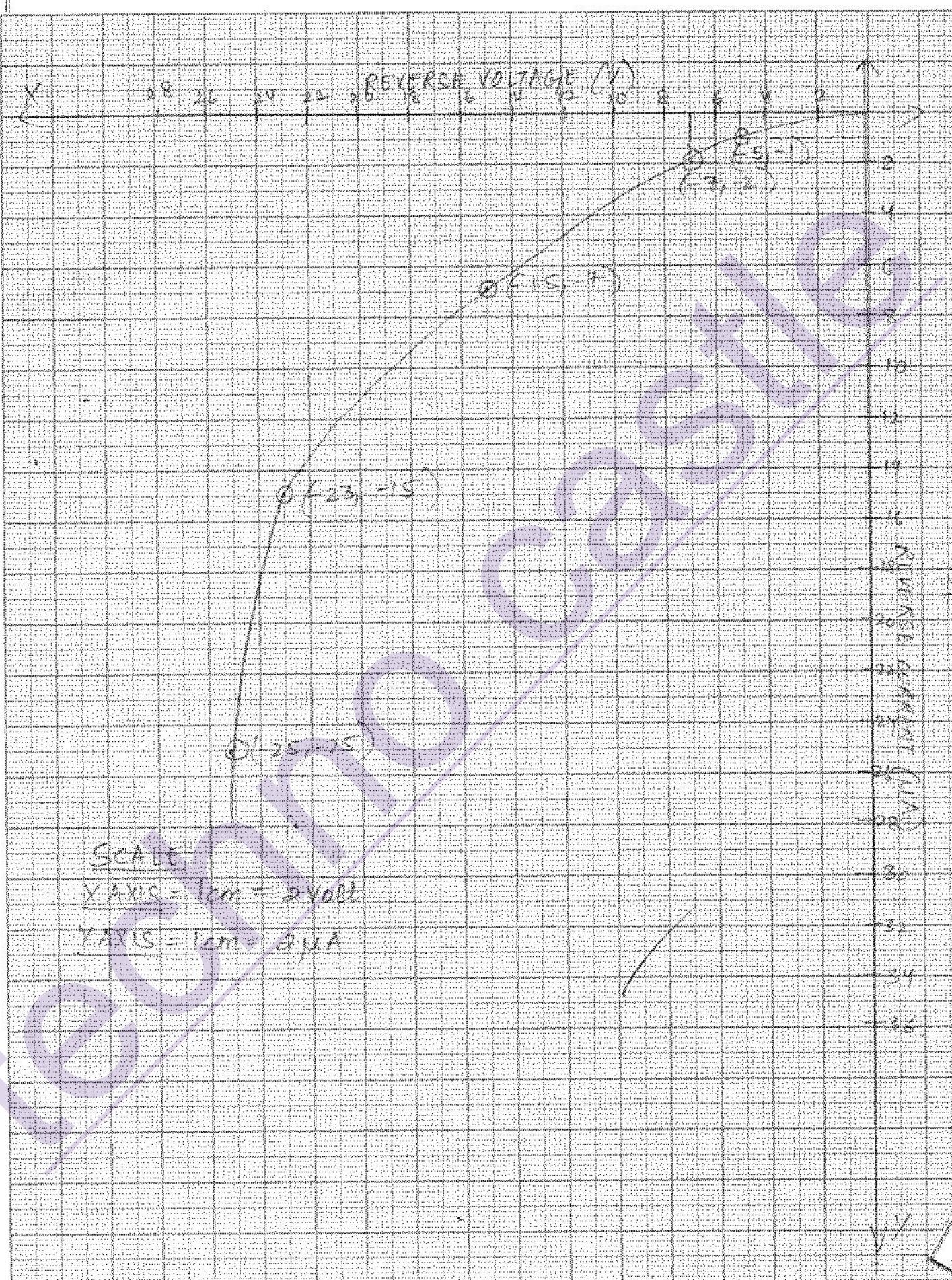

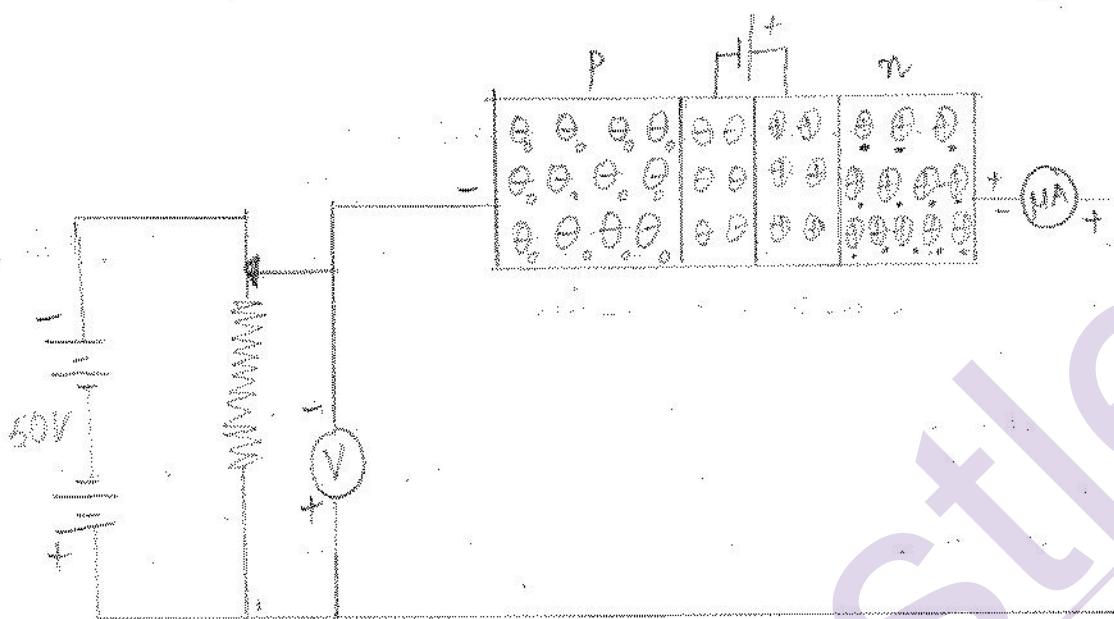

S.NO	VOLTAGE	CURRENT (mA)
1.	0	0
2.	1	2
3.	2	4
4.	3	6
5.	4	8
6.	5	10
7.	6	12
8.	7	14
9.	8	16
10.	9	18
11.	10	20
12.	11	22
13.	12	24
14.	13	26
15.	14	28
16.	15	30
17.	16	32
18.	17	34
19.	18	36
20.	19	38
21.	20	40
22.	21	42
23.	22	44
24.	23	46
25.	24	48
26.	25	50

P-N-JUNCTION UNDER REVERSE BIAS

AIM: To draw I-V characteristic curve of a p-n junction in reverse bias.

APPARATUS: a p-n junction diode, a 3 volt battery, a 50 volt battery, a high resistance rheostat, 0-50V voltmeter, 0-100 μ A ammeter, one way key, sand paper, connecting wires.

THEORY: When p-junction is connected to -ve terminal of battery and n-junction to +ve terminal, it is said to be REVERSE biased. When reverse bias voltage increases, initially there is less increase in current, but when reverse bias voltage increases to sufficiently high value, reverse current increases to large value. This is called zener breakdown voltage.

RESULT: Junction resistance for reverse bias = $2 \times 10^6 \Omega$


PRECAUTIONS:

1. All connections must be neat, clean and tight.
2. Reverse bias voltage beyond breakdown should not be applied.

SOURCES OF ERROR:

1. Junction diode supplied may be faulty.

Teacher's Signature : 

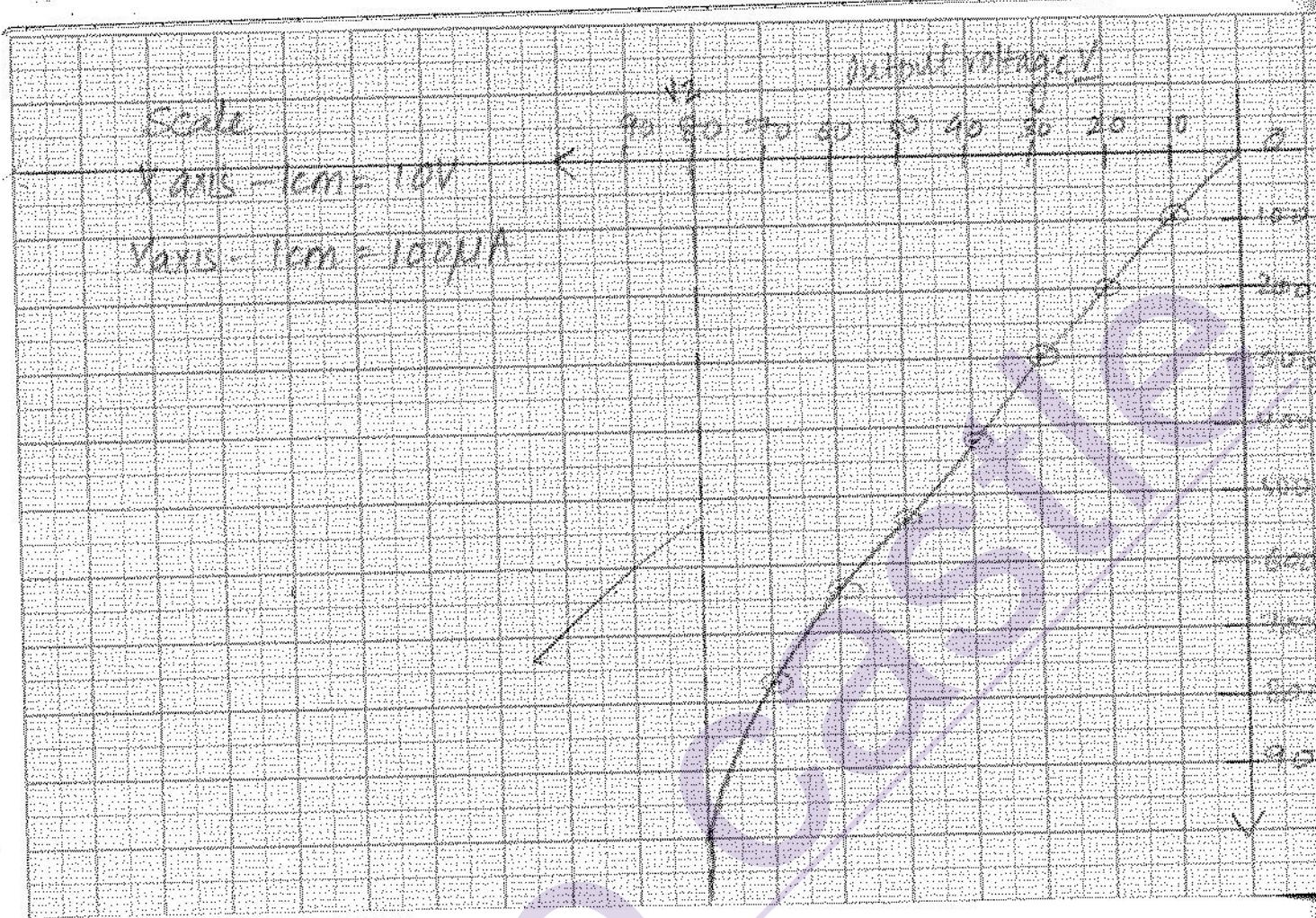

ANGLE	OUTPUT VOLTAGE AC	CURRENT AMP
1	10	100
2	20	200
3	30	300
4	40	400
5	50	500
6	60	600
7	70	700
8	80	800

CHARACTERISTICS OF ZENER DIODE

AIM: To draw the characteristic curve of a zener diode and to determine its reverse breakdown voltage.

APPARATUS : A zener diode ($V_Z = 6V$), 10 V battery, a high resistance rheostat, ammeter, voltmeter, one way key, connecting wires.

THEORY : It is a semiconductor diode, in which the n-type and p-type sections are heavily doped. This results in low value of reverse breakdown voltage (BV_Z). This is called zener voltage.

$$V_o = V_I - R_I I_Z \rightarrow \begin{matrix} \text{input current} \\ \downarrow \end{matrix}$$

$$\begin{matrix} \text{input voltage} \\ \downarrow \\ \text{output voltage} \end{matrix}$$

$$R_I - \text{Input resistance}$$


RESULT:

The reverse breakdown voltage of Zener diode is 80V


PRECAUTIONS:

1. All connections should be neat, clean, tight
2. Key should be used in circuit.

Teacher's Signature : 

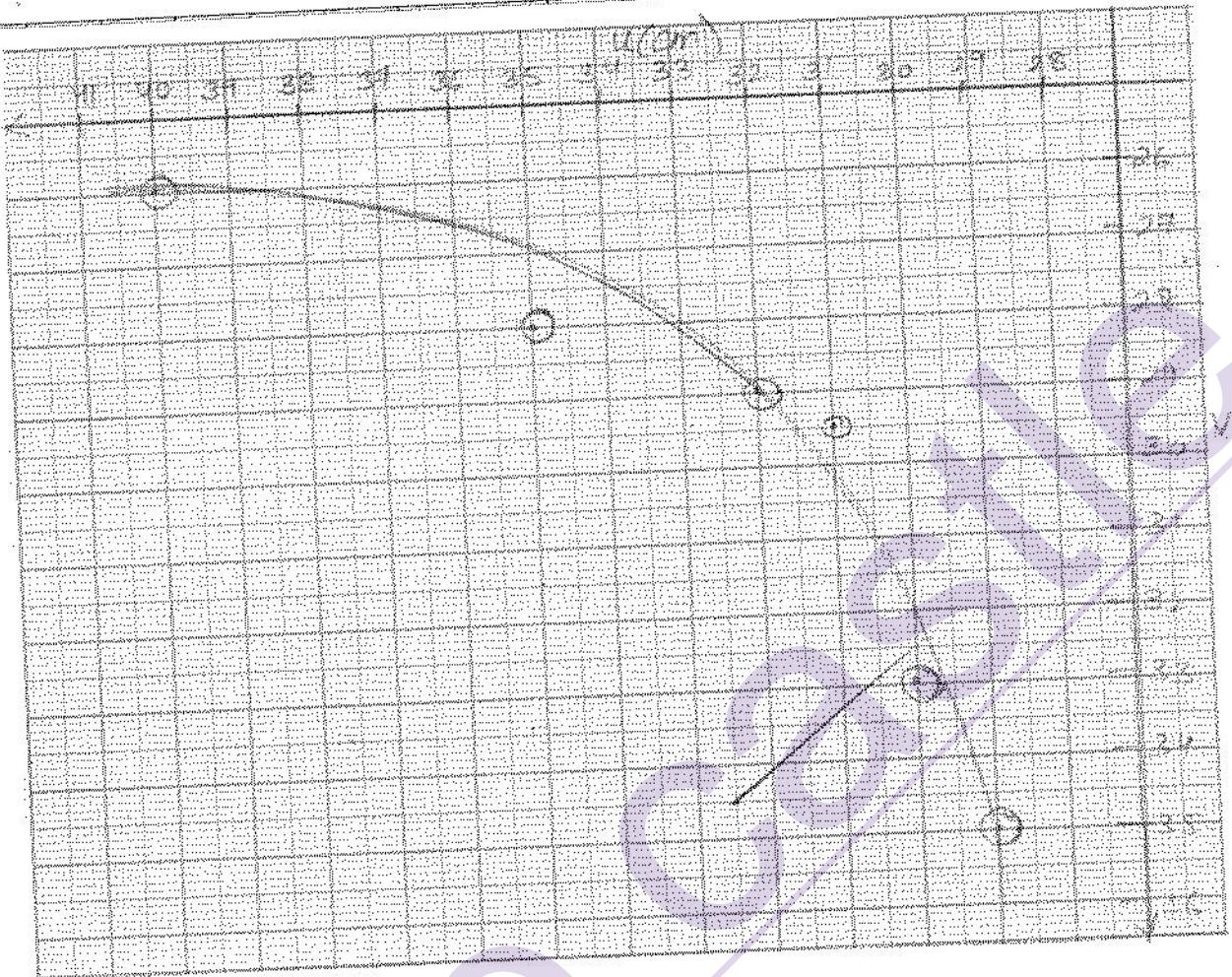

graph b/w ('l' and 'v')

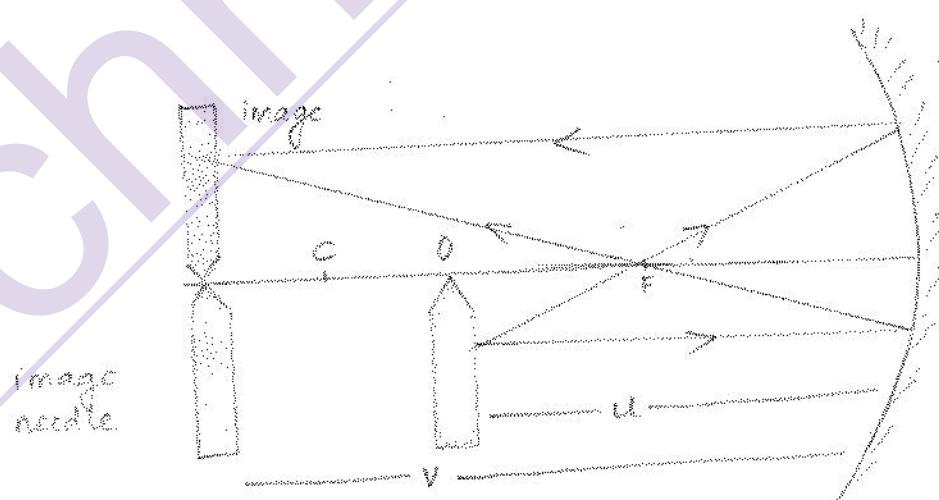

FOCAL LENGTH OF CONCAVE MIRROR

AIM: To find focal length of concave mirror by calculating f for different values of v .

APPARATUS:

An optical bench alongwith 3 uprights, one mirror holder, 2 needles, concave mirror, a knitting needles, metre scale

THEORY:

Formula used

$$\frac{1}{f} = \frac{1}{v} + \frac{1}{u}$$

$$f = \frac{uv}{u+v}$$

f = focal length

v = distance of image from mirror


u = distance of object from mirror

- 1) Plot graph between v and u
- 2) Plot graph between $\frac{1}{v}$ and $\frac{1}{u}$

RESULT:

The focal length of given concave mirror is -15.5 cm

Teacher's Signature :

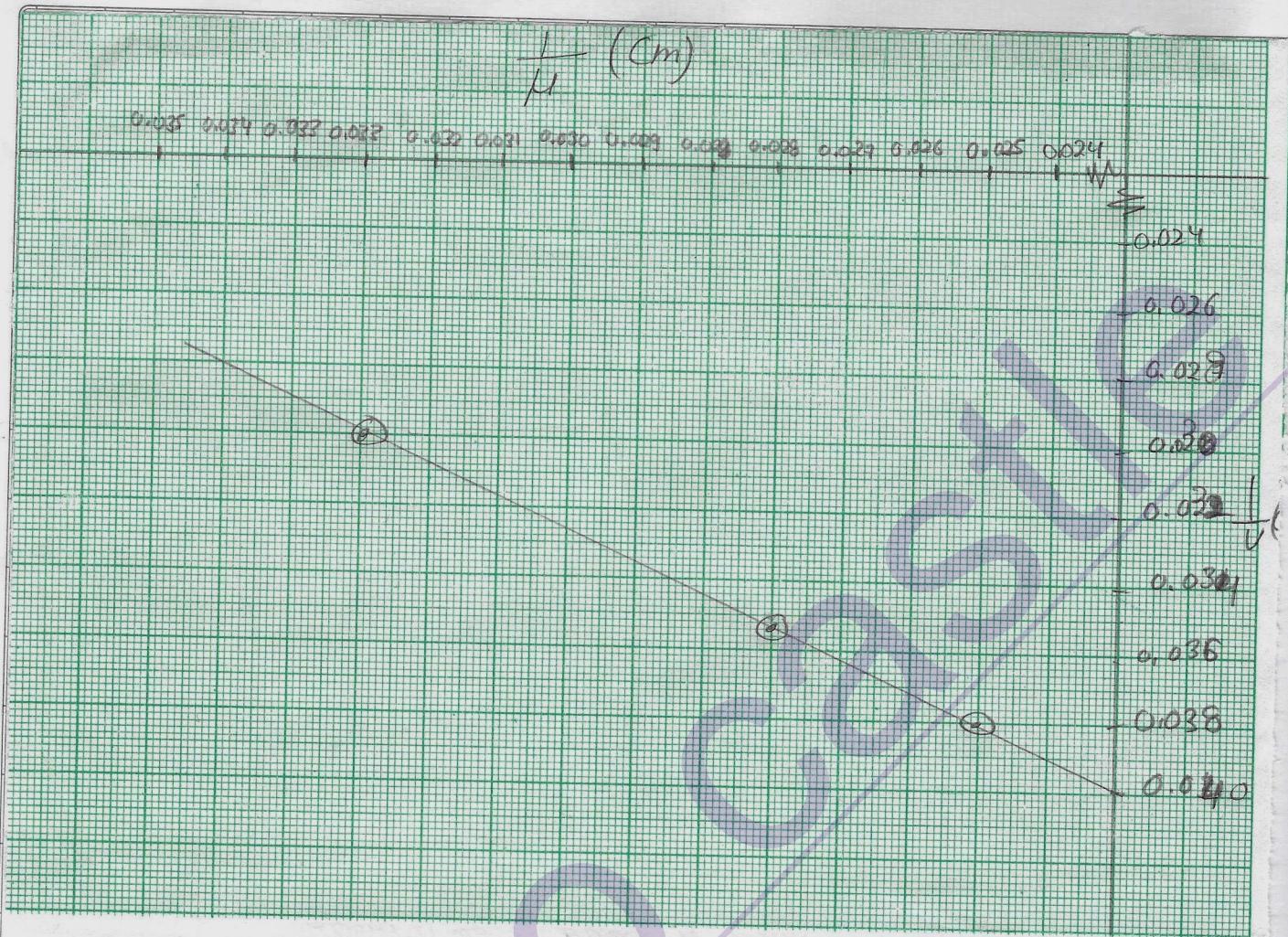

graph $b/w \frac{1}{\mu}$ and $\frac{1}{V}$


S.NO	μ (cm)	V (cm)	$\frac{1}{V}$ (cm ⁻¹)	$\frac{1}{\mu}$ (cm ⁻¹)	$\frac{1}{\mu} = \frac{V}{V+U}$
1	-30	-33	-0.033	-0.030	-15.71
2	-29	-35	-0.034	-0.028	-15.85
3	-35	-28	-0.028	-0.035	-15.55
4	-40	-26	-0.025	-0.038	-15.75
5	-32	-29	-0.031	-0.034	-15.30
6	-31	-29.5	-0.032	-0.033	-15.21

PRECAUTION

The upright should be vertical
Index correction for U & V must be applied

SOURCE OF ERROR

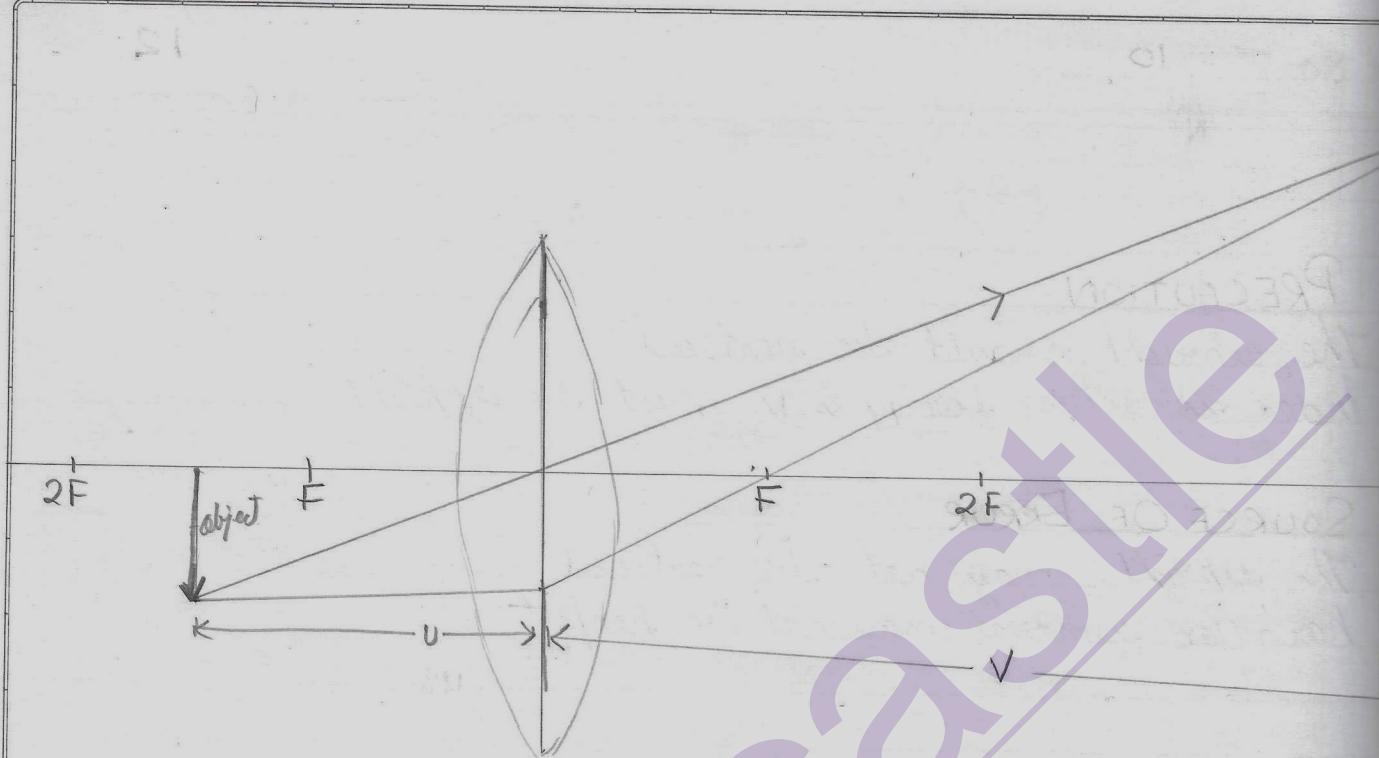
The upright may not be vertical
Parallax removal may not be perfect



	$u(\text{cm})$	$v(\text{cm})$	$y_0(\text{cm})$	$y_1(\text{cm})$	$f = \frac{uv}{u+v}$
1	-40	+43	0.025	0.023	20.
2	-43	40	0.023	0.025	20.
3	-37	47	0.027	0.021	20.
4	-47	37	0.021	0.27	20.



Sir

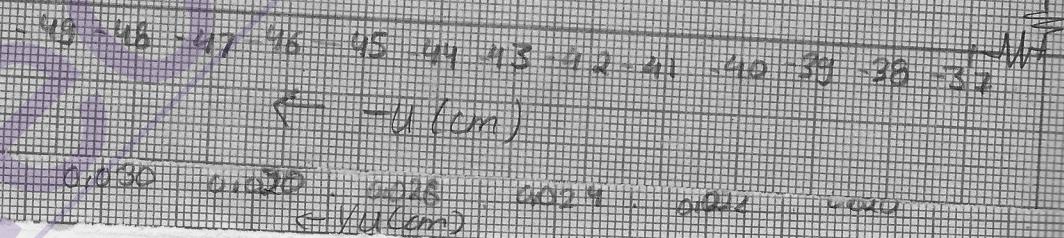

FOCAL LENGTH OF CONCAVE MIRROR

AIM To find focal length of a concave lens & find different values of v for different value of u

APPARATUS

An optical bench, with 3 upright, a concave lens with lens holder 2 optical needle, a half metre scale, a knitting needle

THEORY

Formula Used

$$\frac{1}{f} = \frac{1}{v} - \frac{1}{u}$$

$$f = \frac{uv}{u-v}$$

f = focal length

u = objective distance

v = image distance

RESULT

The focal length of lens = 20.95 cm

PRE CAUTION



Tips of object and needle be should lie at same height as the centre of lens

- Index correction for u & v must be applied

Source Of Error

Upright may not be vertical

Polar removal may not be perfect

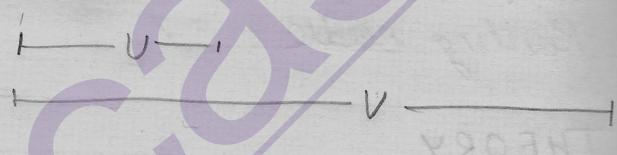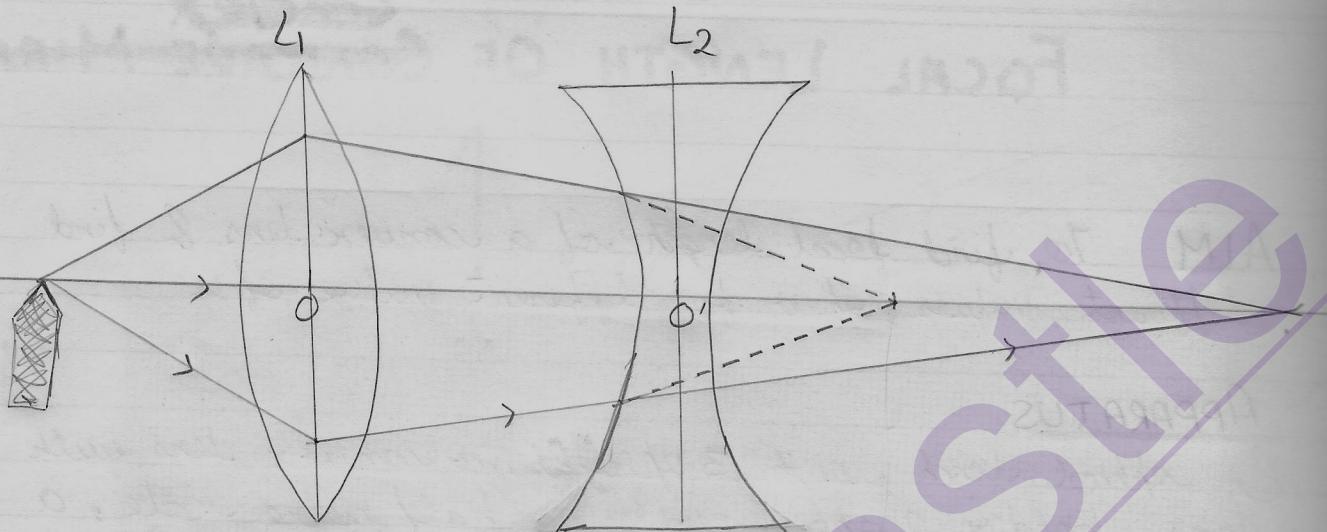

S.no	$U(\text{cm})$	$V(\text{cm})$	$f(\text{cm})$
1	10cm	20cm	-20cm
2	12cm	31cm	-19.8 cm
3	15cm	59cm	-20.2 cm
4	11.1cm	25cm	-20 cm

FOCAL LENGTH OF CONCAVE LENS

AIM: To find focal length of a concave lens using a convex lens

Optical bench, 4 upright, convex lens, concave lens, lens holder, 2 optical needles, half meter scale, knitting needle

$$\frac{1}{f} = \frac{1}{v} - \frac{1}{u}$$

$$f = \frac{uv}{u-v}$$

f = focal length

u = objective distance

v = image distance

focal length of concave lens is - 20 cm

The lens must be clean

Focal length of concave lens should be less than
1 of concave lens

Parallax removal may not be perfect
so upright may not be verified vertical.


2. Index correction for u and v must be applied.

SOURCES OF ERROR:

1. The uprights may not be vertical
2. Parallax removal may not be perfect.

8

Teacher's Signature :

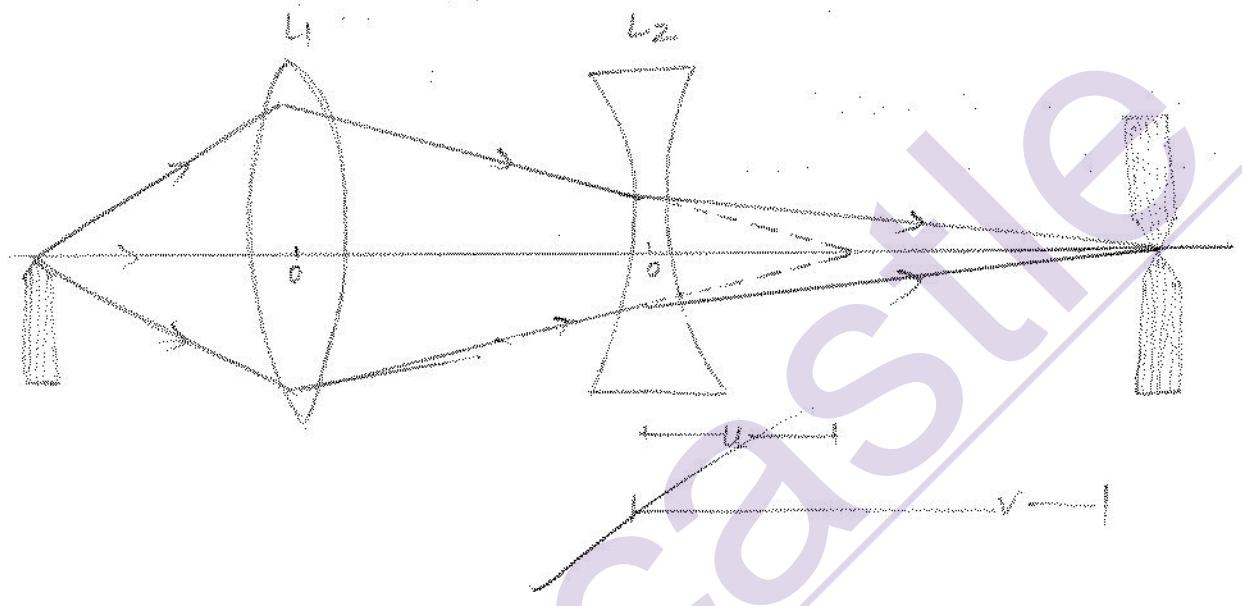

SIDE	u(cm)	v(cm)	w(cm)
AB	10cm	20cm	- 20cm
BC	12cm	31cm	- 19.8cm
CA	15cm	59cm	- 20.2cm
DA	14.1cm	25cm	- 20cm

FOCAL LENGTH OF CONCAVE LENS

AIM: To find focal length of a concave lens using a convex lens.

APPARATUS: optical bench, Uprights, convex lens, concave lens, lens holders, 2 optical needles, half metre scale, knitting needle.

THEORY:

$$\frac{1}{f} = \frac{1}{v} - \frac{1}{u}$$

$$f = \frac{uv}{u-v}$$

f = focal length

u = object distance

v = image distance

RESULT:


focal length of concave lens is - 20 cm


PRECAUTIONS:

1. The lens must be clean.
2. focal length of concave lens should be less than f of concave lens.

SOURCES OF ERROR

1. Parallax removal may not be perfect.
2. The uprights may not be vertical.

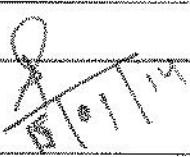Teacher's Signature : 

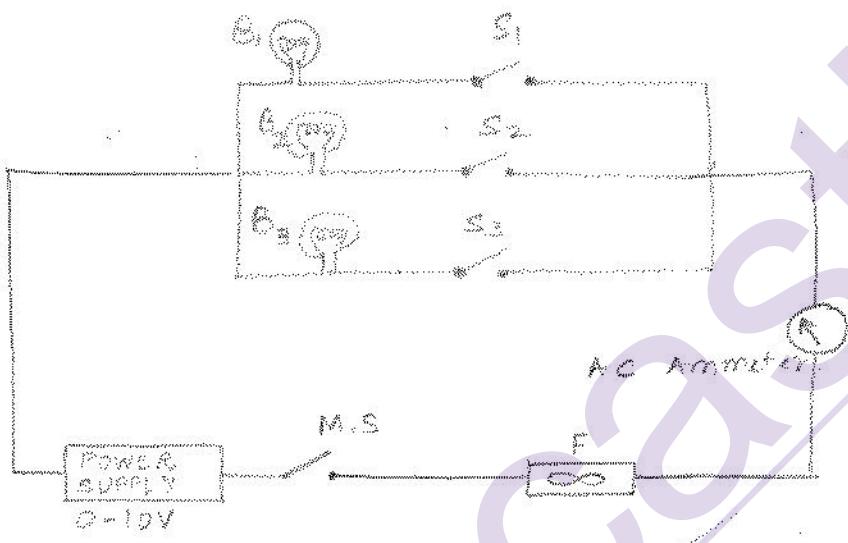

ACTIVITY 1

AIM: To assemble a household circuit, comprising three bulbs, switches, fuse and a power source.

APPARATUS: Bulbs, fuse, battery, fuse wire

THEORY: Formula used for calculating Power

$$P = \frac{V^2}{R} = I^2 R = VI$$

$$P_{\text{net}} = P_1 + P_2 + P_3 + \dots + P_n$$


PROCEDURE:

- 1) Connect the bulbs B_1, B_2, B_3 in series with switches S_1, S_2 and S_3 resp and connect each set of $B-S$ in parallel with each other.
- 2) Connect main supply to a step down transformer to get required voltage from 0 - 10V
- 3) Connect the main fuse MS in series with the power supply
- 4) Connect an A.C. ammeter in series with the $B-S$ set.
- 5) Connect one end of power supply to one end of $B-S$ set
- 6) Check the circuit one again to ensure that household circuit is complete.
- 7) Gradually increase the current to 0.75A, the fuse burns at 0.6A.

X X X X

Teacher's Signature

Jeh

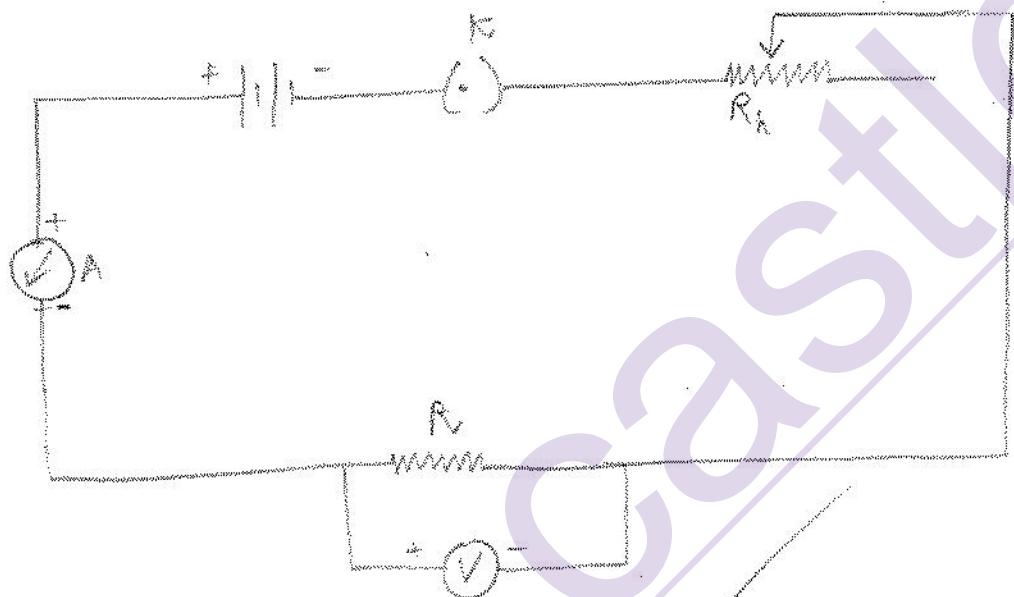

techno castle

ACTIVITY

AIM: To assemble the components of a given electrical circuit

APPARATUS: voltmeter, ammeter, battery, a rheostat, connecting wires, sand paper, resistance coil


PROCEDURE:

- 1) connect the components as shown in fig.
- 2) connect the ammeter in series with circuit.
- 3) connect voltmeter in parallel to resistor.
- 4) connect switch in series with battery.
- 5) assemble all components and circuit is complete.

UTILITY: It is used for measuring unknown resistance.



Teacher's Signature :

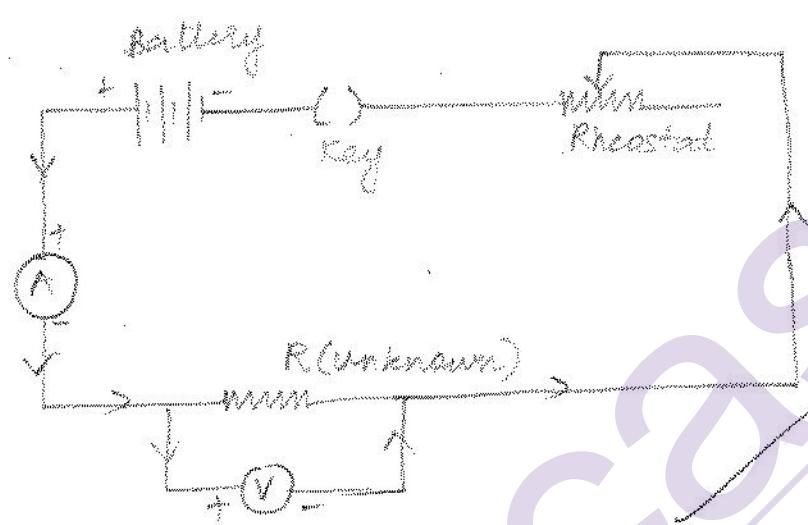

ACTIVITY 3

AIM: To draw the diagram of a given open circuit comprising at least a battery, resistor, key, ammeter and voltmeter.

APPARATUS: battery eliminator, rheostat, resistance box, key, ammeter, voltmeter

THEORY: An open circuit is combination of primary components of electric circuit in such a manner that on closing the circuit no current is drawn from the battery.

PROCEDURE:

Ammeter: to be connected in series with the dominator

Voltmeter: to be connected in parallel to resistor

Rheostat: connected in series with eliminator.

Resistance coil: connected in parallel

One way key: connected in series to battery eliminator

Connect components correctly as per circuit diagram

Teacher's Signature : _____

ACTIVITY 4

AIM: To study the nature and size of the image formed by a concave mirror on a screen by using a candle and a screen.

APPARATUS: Optical bench, three uprights, concave mirror, holder, candle, card board screen.

THEORY:

$$\frac{1}{v} + \frac{1}{u} = \frac{1}{f}$$

$$u = \infty$$

$$v = -f$$

$$u = -2f$$

$$v = -2f$$

$$u = -f$$

$$v = \infty$$

PROCEDURE: Find rough focal length of concave mirror by usual method.

- 1) Mount the concave mirror, screen and candle as shown.
- 2) Adjust the mirror to get inverted, erect image of candle on screen.
- 3) As the object is moved towards the mirror, the image gets enlarged slowly. Then after reaching a distance equal to f , no image is seen.
Thus focal length can be measured.

Teacher's Signature :

ACTIVITY 5

AIM: To observe diffraction of light through a thin slit between sharp edges of razor blade.

APPARATUS: 2 razors blades, adhesive tapes, monochromatic lights, black paper, glass plate
formula used

$$\sin\theta = \frac{n\lambda}{d}$$

d = width of slit

θ = angle of diffraction

n = order of diffraction

λ = wavelength of light

PROCEDURE:

- 1) Fix the black paper on glass plate using adhesive
- 2) place 2 razor blades so that their sharp edges are parallel and extremely close to each other to form a narrow slit by them.
- 3) Throw a beam of light on the slit by laser pencil
- 5) A diffraction pattern of alternate bright and dark bands is seen on the wall

CONCLUSION:

When light waves are incident on a slit or aperture then it bends away at corners of slit showing the phenomena of diffraction of light.

Teacher's Signature : _____

POWER

FOCAL LENGTH

P ₁	P ₂	f ₁	f ₂
2	8	50cm	12.5cm
4	6	25cm	16.7cm
5	5	20cm	20cm

ACTIVITY VI

AIM: To obtain a lens combination with the specified focal length by using 2 lenses from given set of lenses.

APPARATUS: lenses, lens holder, stand, metre scale

THEORY:

$$\frac{1}{f} = \frac{1}{f_1} + \frac{1}{f_2} \quad (f = \text{focal length})$$

$$P = P_1 + P_2 \quad (P = \text{power})$$

PROCEDURE: Keep the white painted vertical wooden board to serve as a screen.

- 1) The convex lens fixed into a holder is moved towards left of screen and then right to get sharp image.
- 2) The lens is moved towards and away from the screen till a sharp image is formed.
- 3) Then use second lens and find focal length
- 4) Calculate power using 'f'

X X X

Teacher's Signature :

ACTIVITY 7

AIM: To observe polarisation of light using two polaroids.

APPARATUS: Thin glass slab, monochromatic light, polaroid

THEORY: When an unpolarised is made to incident on interface of 2 transparent media at polarising angle, refracted and reflected rays are at 90° .

PROCEDURE:

- 1) Keep a thin glass sheet in a horizontal plane surface with a hole under sheet.
- 2) Take a beam of monochromatic light having parallel rays and make it incident on upper face of glass sheet.
- 3) Adjust the angle of incidence to 57.5°
- 4) Observe reflected and refracted ray. They are \perp to each other.

RESULT:

When the two polaroids are \parallel to each other, transmitted light is passed through it. But when they are \perp , there is no transmitted light. The light has transverse nature.

Teacher's Signature : 