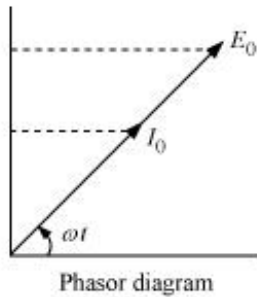


Alternating Current

AC through a resistor:

- When AC flows through a resistor, the voltage and current are in phase with each other.




AC through an inductor:

- The alternating emf is ahead of alternating current by a phase angle of $\frac{\pi}{2}$.

Inductive reactance (X_L):

$$X_L = \omega L = 2\pi fL$$

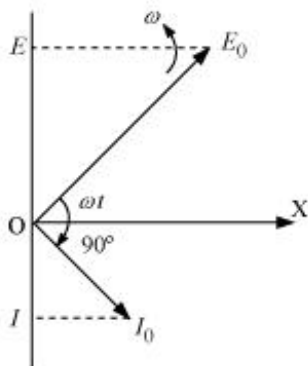


AC through a capacitor:


- The current leads the emf by a phase angle of $\frac{\pi}{2}$.

Capacitive reactance (X_C):
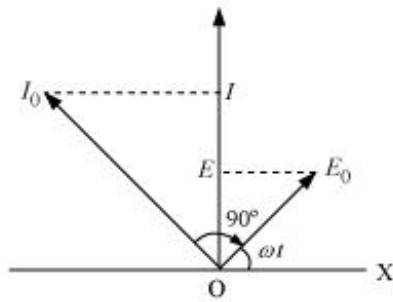
$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$



- **AC through *LCR* series circuit:**

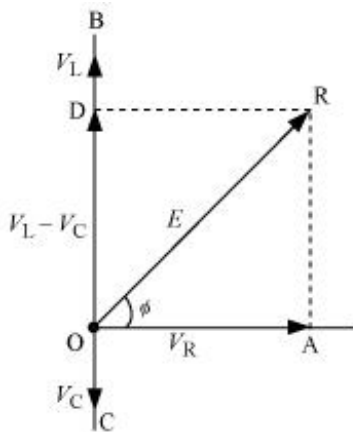

$$E = I\sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \Phi = \frac{X_L - X_C}{R}$$

Impedance (Z):

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

- **Power in *LCR* circuit:**

$$P_{av} = \frac{E_v^2 R}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\text{Power factor} = \cos \Phi = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

Resonance

- It is the property exhibited by an LCR circuit.
- At a certain frequency known as resonating frequency (ω_0) the current through the circuit is maximum.
- It occurs at the frequency that can make $X_L = X_C$ or $\omega L = \frac{1}{\omega C}$.

- Impedence of the circuit $Z = R$.
- resonating frequency $\nu = \frac{1}{2\pi\sqrt{LC}}$
- Quality factor, $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$ is used to measure the sharpness of the resonance.

Power in AC circuit

- In AC circuit the power is given as $P = VI\cos\phi$
 - where, V = rms value of the voltage
 - I = rms value of the voltage
 - $\cos\phi$ = power factor = $\frac{\text{true power}}{\text{apparent power}}$
 - $\phi = \tan^{-1}\left(\frac{X_C - X_L}{R}\right)$
- Cases for power factor
 - For purely resistive circuit $\cos\phi = 1$, $\phi = 0$
 - For purely capacitive circuit $\cos\phi = 0$, $\phi = \frac{\pi}{2}$
 - For purely inductive circuit $\cos\phi = 0$, $\phi = -\frac{\pi}{2}$

LC Oscillations

- When capacitor of capacitance C charged to and inductor of inductance L are connected then:
 - energy stored in C oscillates between L and C .
 - energy of the oscillations is given by $\nu = \frac{1}{2\pi\sqrt{LC}}$.
 - Total energy in L and C every instant remains constan.
- A transformer consists of an iron core, on which are bound a primary coil of N_P turns and a secondary coil of N_S turns. If the primary coil is connected to an AC source, the primary and secondary voltages are related by

$$V_s = \left(\frac{N_s}{N_p}\right) V_p$$

And the currents are related by

$$I_s = \left(\frac{N_p}{N_s}\right) I_p$$

If $N_S > N_P \rightarrow$ The voltage is stepped up *step – up transformer*

If $N_S < N_P \rightarrow$ The voltage is stepped-down *step – down transformer*

